

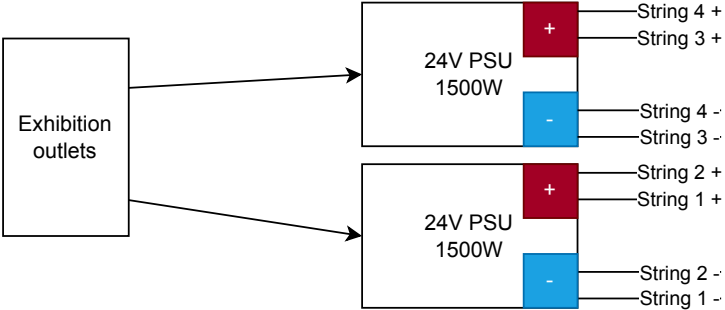


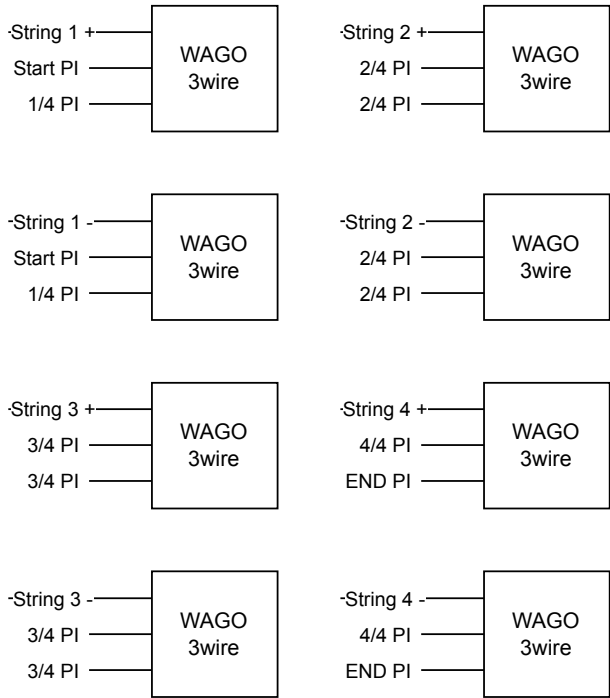



PI = Power Injection

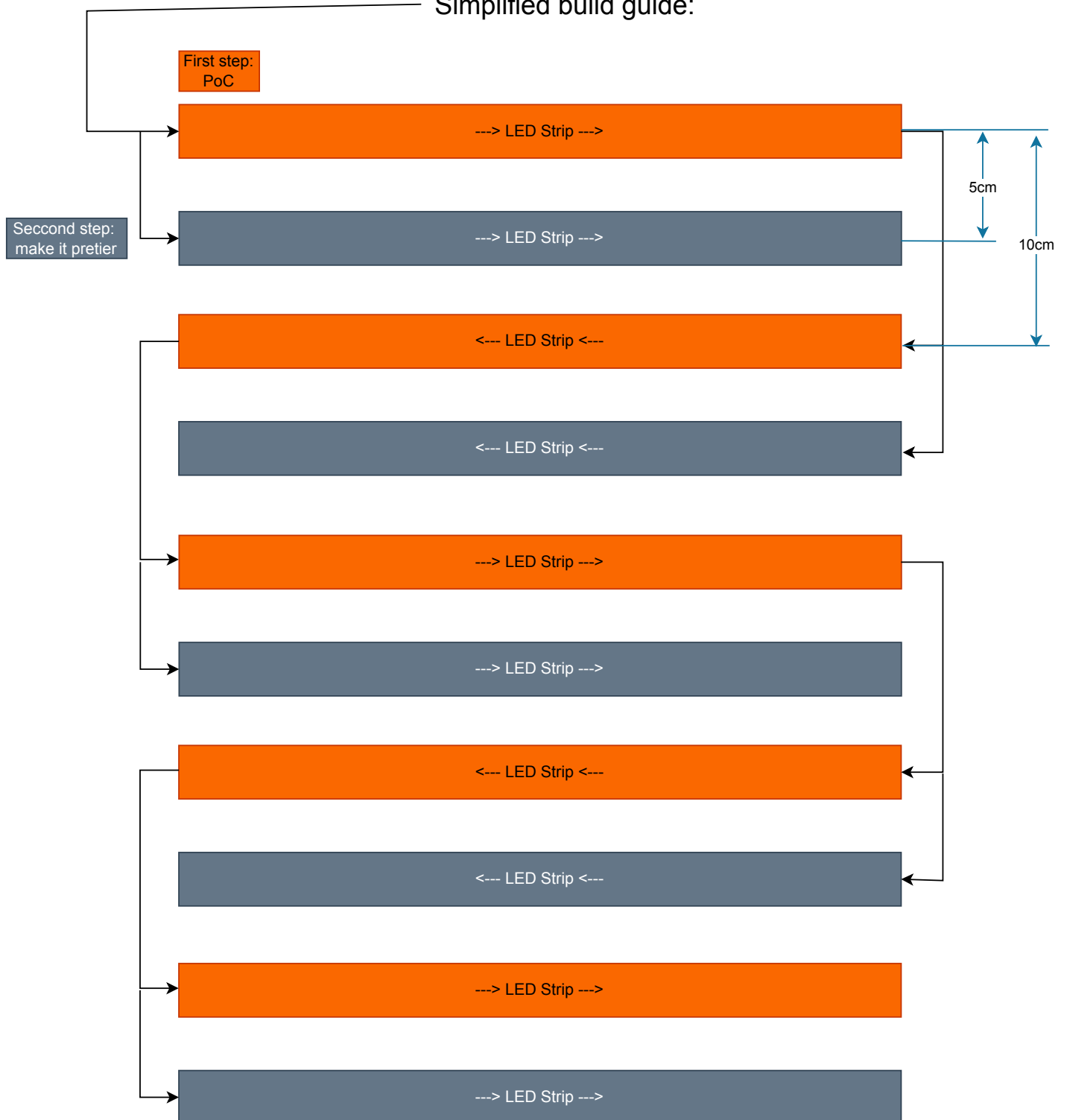

Simplified build guide:



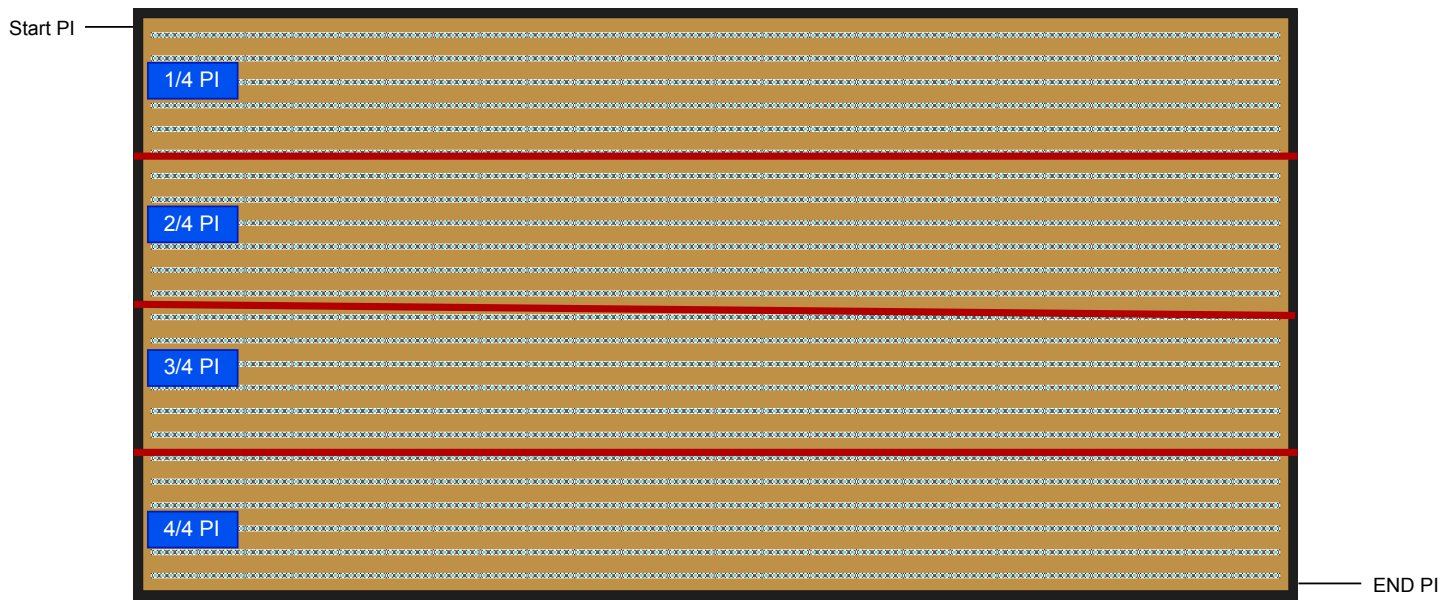

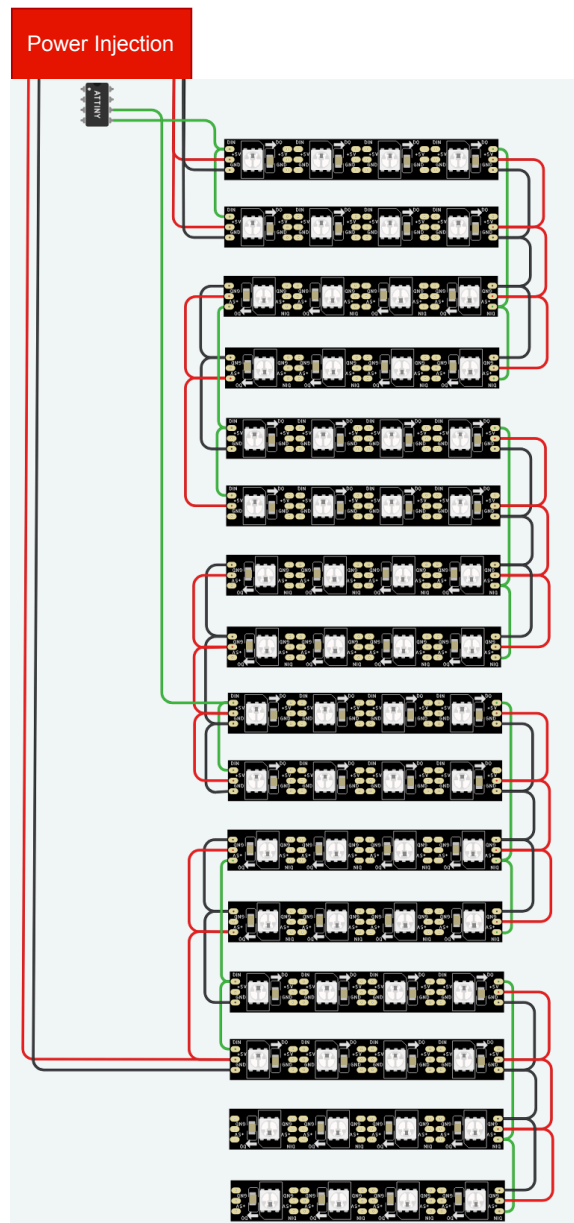

Text definition: (Yapping is normal in electrotechnics)

The LED strips will be all wired in parallel with even power injection. For now I see the need for 8 Power injections along the way, but we'll find out later when we wire all the LED strips in series and then we can worry about power injections.

The LED strip wiring is interesting, as there will be two strips wired in parallel and they will share the same pixel mapping because of they're wired in parallel. Then it will go to the two strips below and etc.

And in the middle we have to have another GPIO from TwinkleTron for the bottom rows as I don't think the signal would be suitable as this point.

Almost every wire is going on the backside, with local connections being on the front side, That's also true for BCB's lol.